



Drive a 7-Segment LED with an Arduino

Written By: Riley Porter



TOOLS:

- [Arduino microcontroller \(1\)](#)




PARTS:

- [misc resistors \(2\)](#)
[Close to 220 Ohms is good enough.](#)
- [Mini breadboard \(1\)](#)
- [Connecting \(jumper\) wires \(11\)](#)

SUMMARY

Using the Arduino development platform you will learn how to display numbers and letters on a single 7-segment LED display. There are many ways to drive 7-segment displays, and this is a fairly simple method. However, using this method to drive even one LED 7-segment array "burns" (occupies) many of the digital I/O pins on your Arduino. In later projects, I'll show you how to use a dedicated 7-segment LED driver.

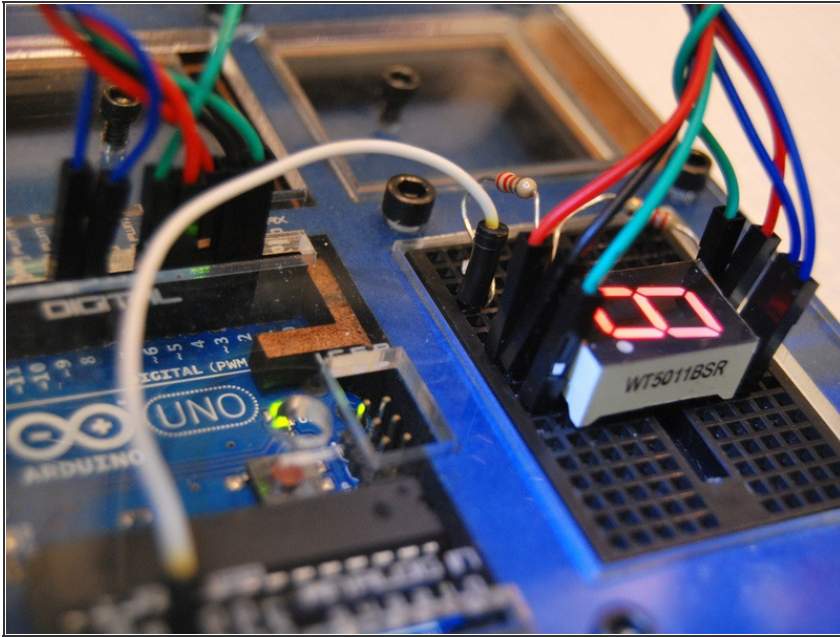Step 1 — Drive a 7-Segment LED with an Arduino



- Gather up your gear:
 - Two 220-ohm resistors (close to that value is good enough)
 - 11 male-to-male jumper wires
 - 1 Breadboard
 - 1 Arduino Development Board

Step 2



- Wire up your segment. Use the Fritzing image as your guide.
 - A = 8, B = 9, C=2, D=3, E=4, F=5, G=6
 - The two middle pins (Pin 3 and Pin 8) on top and bottom go to Ground (or to the first leg of the 220 ohm resistor). These are our current-limiting resistors.

Step 3

```
Arduino IDE - _7_segment | Arduino 0022
_7_segment 5
// Project: How to drive a 7 segment LED
// By: Riley Porter
// This is an introduction on how to drive a 7 segment LED using only an Arduino. This is
// not the best way to do this. This is meant to be a learning exercise. In later tutorials
// I will show you how to use an dedicated IC using SPI or a Shift Register. Enjoy.

//
#define A 0
#define B 9
#define C 2
#define D 3
#define E 4
#define F 5
#define G 6

void clr()
{
  //Clears the LED
  digitalWrite(A, HIGH);
  digitalWrite(B, HIGH);
  digitalWrite(C, HIGH);
  digitalWrite(D, HIGH);
  digitalWrite(E, HIGH);
  digitalWrite(F, HIGH);
  digitalWrite(G, HIGH);
}

void char_A()
{
  digitalWrite(D, HIGH);
  digitalWrite(C, LOW);
  digitalWrite(F, LOW);
  digitalWrite(E, LOW);
  digitalWrite(A, LOW);
  digitalWrite(B, LOW);
  digitalWrite(G, LOW);
}

void char_B()
{
  //Display 8
  digitalWrite(D, LOW);
  digitalWrite(E, LOW);
  digitalWrite(F, LOW);
  digitalWrite(A, LOW);
  digitalWrite(B, HIGH);
  digitalWrite(G, HIGH);
}

Auto Format finished.
Binary sketch size: 3654 bytes (of a 32256 byte maximum)
```

- Load the code and you're good to go:
 - Get the code from here:
<http://bit.ly/ia3lv7>
- If you copy and paste the code into your Arduino sketch, you will see that if everything is hooked up correctly, it will loop from A-F then 1 - 0. This is not the most interesting project. However it does lay the groundwork for displaying data on a 7-segment LED for your Arduino projects.
- The approach we used to drive this one 7-segment LED took 8 of our digital I/O lines. This is quite a few lines to "burn" for this functionality. However in upcoming tutorials, I will post some more elegant ways to drive 7-segment displays than using 8 digital I/O lines.
- In the code there are 15 functions that will display the letter or number represented by the function name on the LED display. For example, if you were to run `seven()`, this would display the number 7 on the display. If you write a Pin LOW, you are in fact turning on that LED. If you write a pin HIGH it is now turned off.
- That's it! All you have to do now is to program it to display something useful for your project.

